

Name and Std No.: Riley Lawson 116555487 Lab Section: 6

Date: 10/29/2020

Submission Instructions:

Prelab:

1. Complete the prelab
2. Submit this report with the prelab completed to Canvas before your lab starts


Lab:

1. Complete the lab according to the instructions
2. Take screenshots of your ModelSim waveform (note: to receive points your NetID has to be present in the screenshot) and insert them into this document.
3. Include screenshots of any related block design files or Verilog files in the report
4. Complete this report and reupload it to Canvas


PRELAB:

Refer to Chapter 5 in your textbook and the lab instructions to complete your pre-lab. Please read all the material and complete the circuit diagrams before you come to the lab.

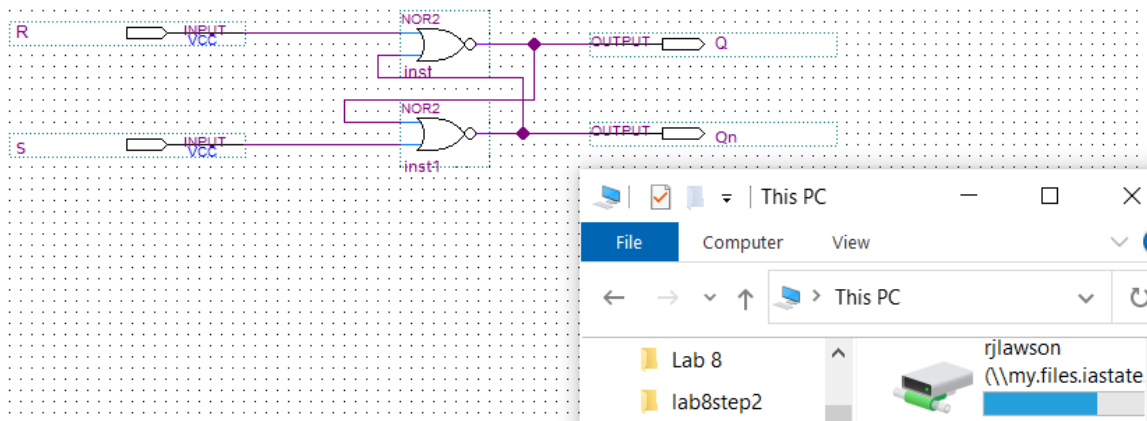
Q1. Draw the circuit diagram for the SR Latch using NOR Gates for **Section 2.0** in the space below.



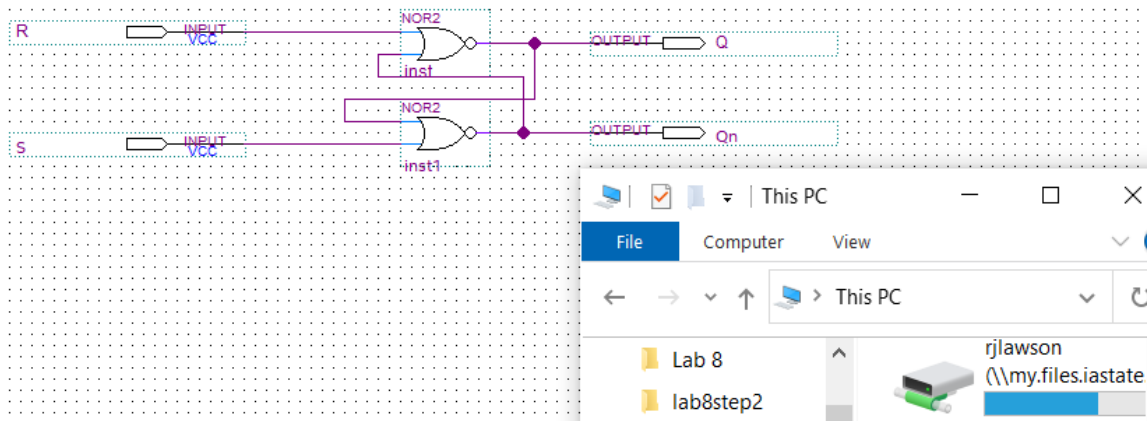Q2. Draw the circuit diagram for the $\overline{S}\overline{R}$ Latch using NAND Gates for **Section 2.0** in the space below.




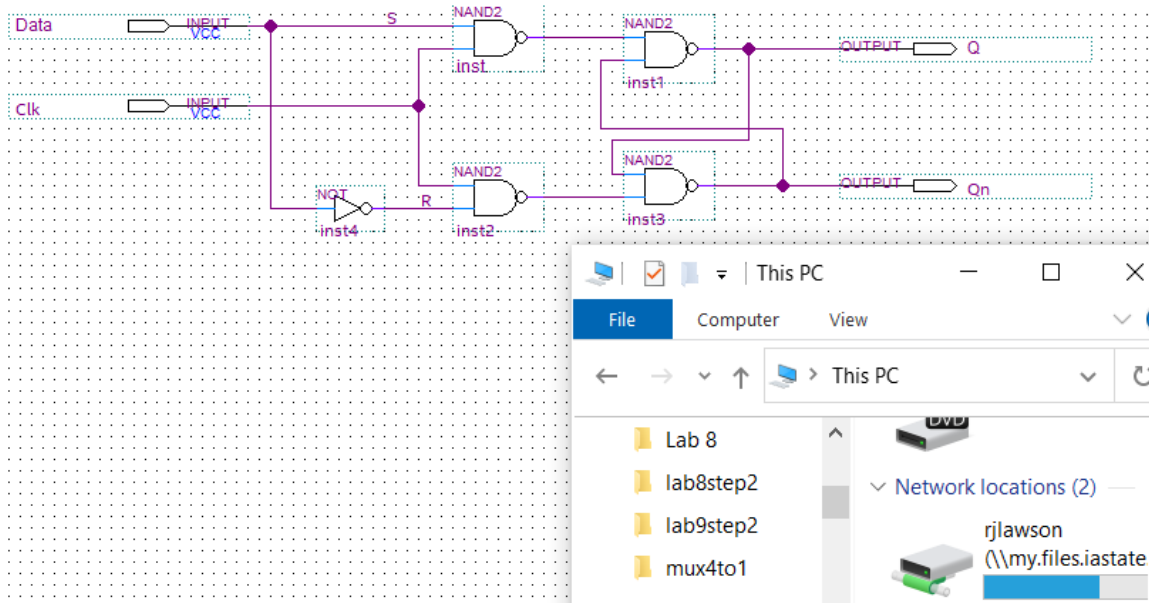
Q3. Draw the circuit diagram for the D Latch using NAND Gates and a NOT gate for **Section 3.0** in the space below.



Q4. Draw the circuit diagram for the Master-Slave D Flip-Flop for **Section 4.0** using the D latches you built in the previous step in the space below. The flip-flop should be triggered by the negative edge of the clock.


FIXED!

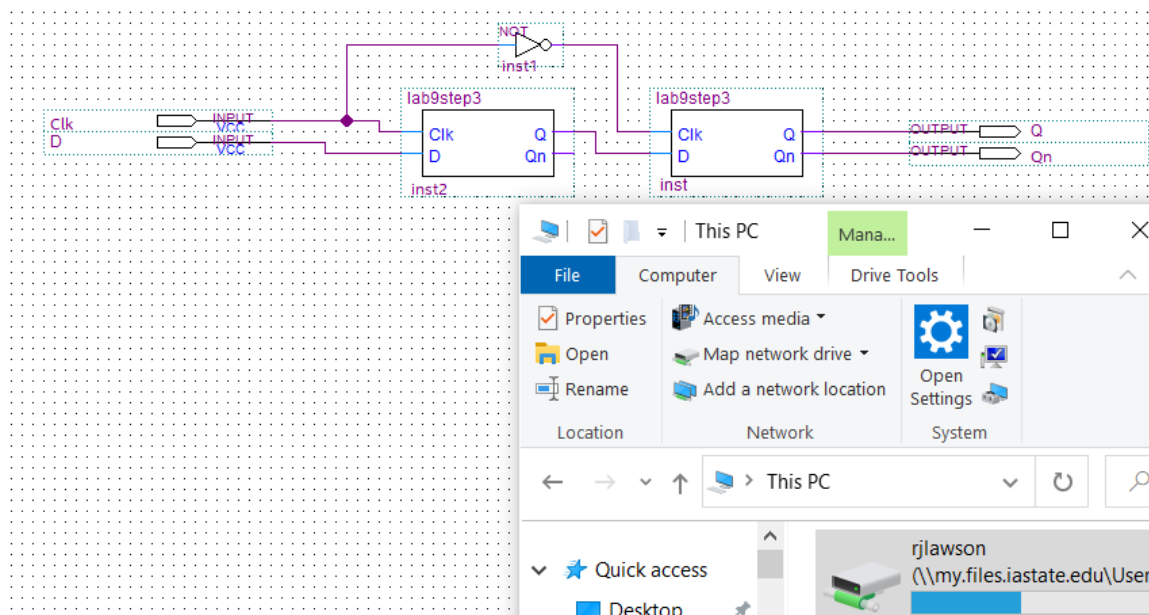

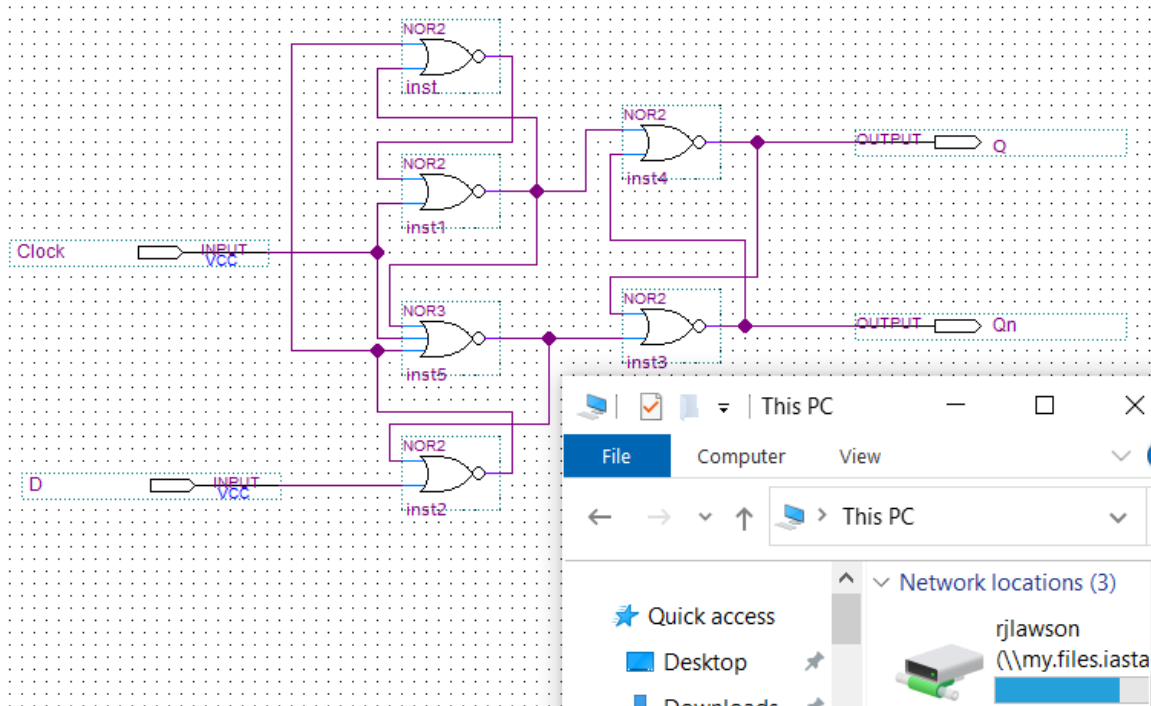

Q5. Draw the circuit diagram for the Positive-Edge-Triggered D Flip-Flop using NAND gates for **Section 4.0** in the space below.

FIXED!

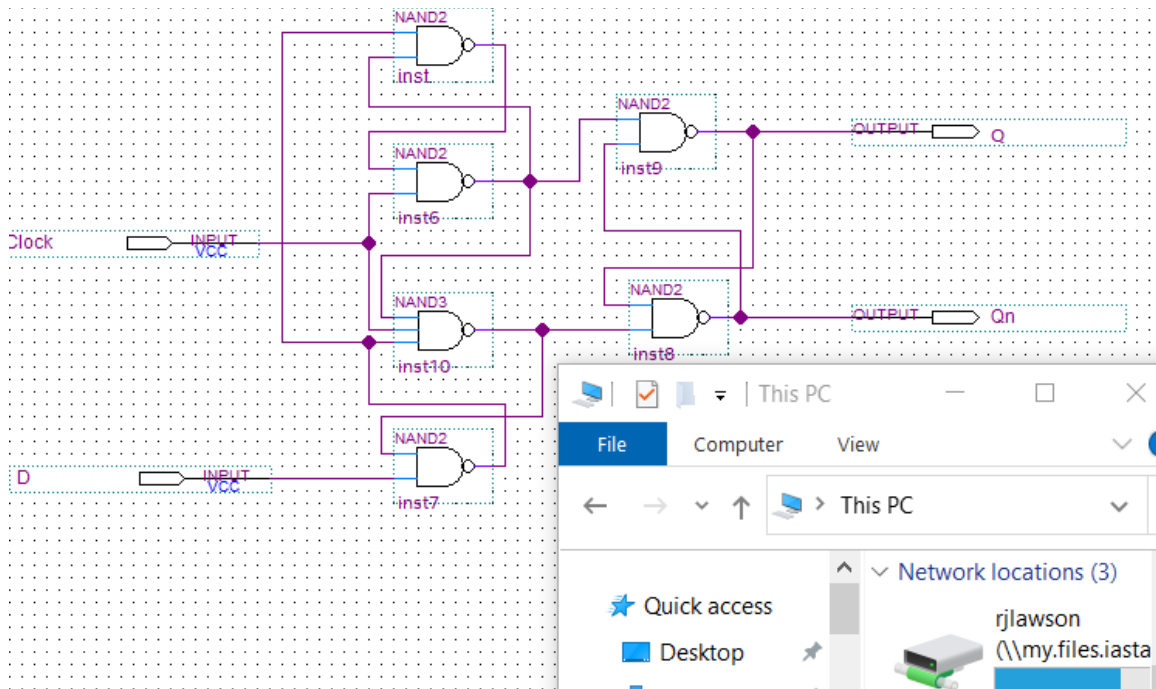

LAB:


2.0 Complete the characteristic table for both versions of the SR latch. Do both versions function properly as a latch?

SR NOR Latch		
S	R	Action
0	0	Keep State
0	1	$Q = 0$
1	0	$Q = 1$
1	1	Restricted Combination


SR NAND Latch		
S	R	Action
0	0	Keep State
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Restricted Combination

NOR Screenshots:
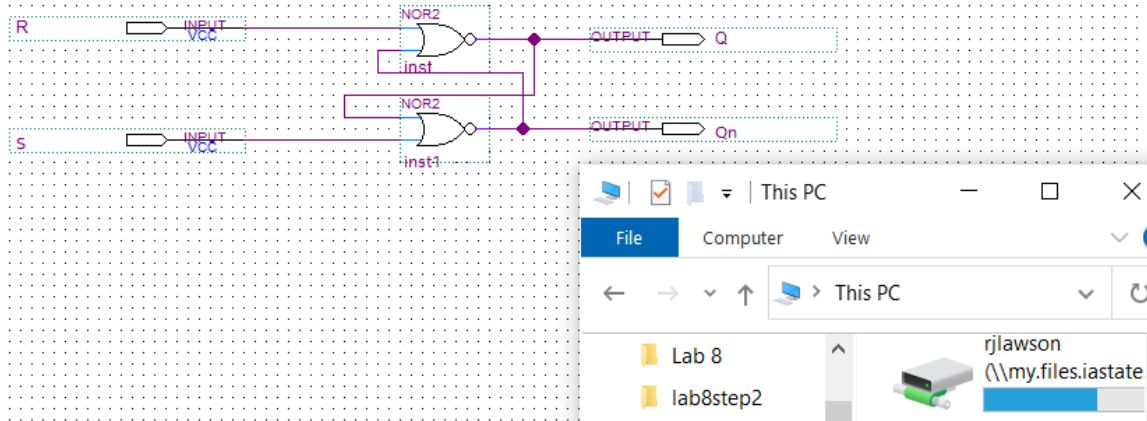
<<<Insert a screenshot of your SR NOR latch here>>>



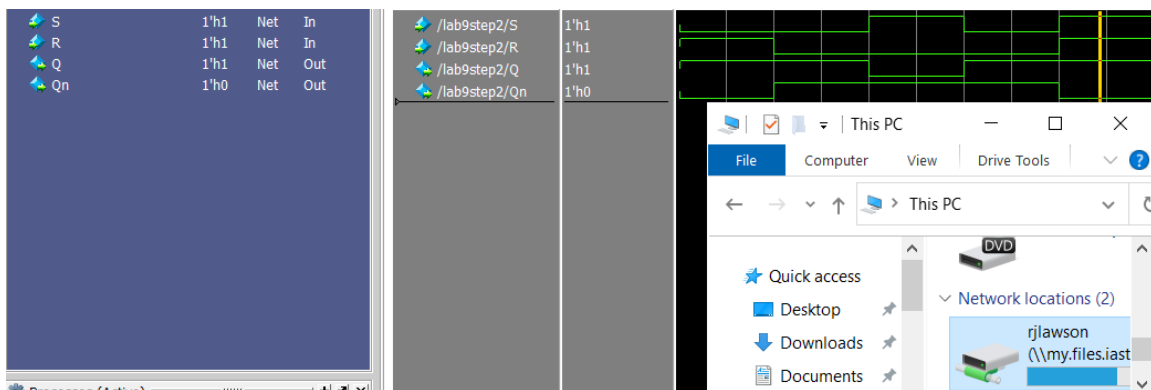
<<< Insert a screenshot of your waveform for your SR NOR latch here>>>




NAND screenshots:

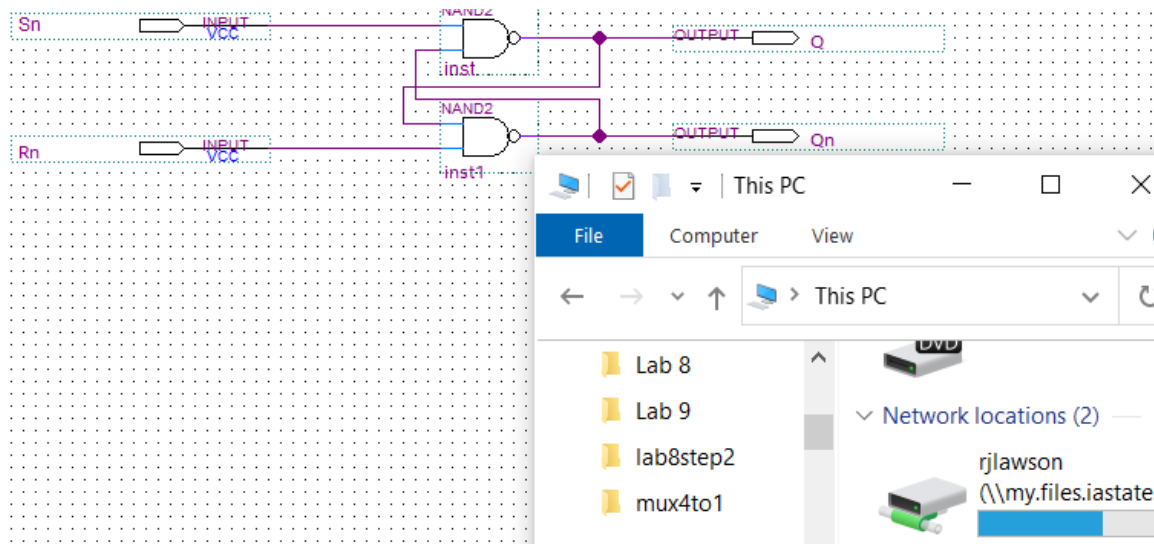
<<<Insert a screenshot of your SR NAND latch here>>>


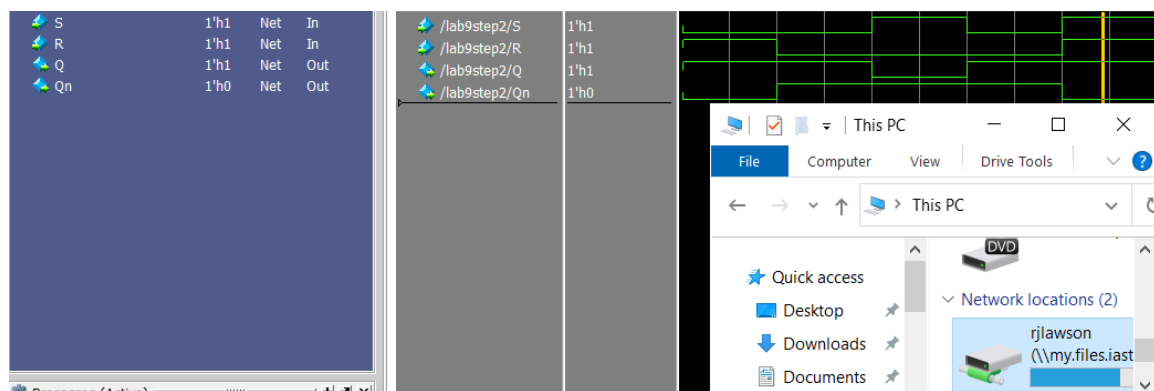
<<< Insert a screenshot of your waveform for your SR NAND latch here>>>



 
3.0 Complete the timing diagram below for your Gated D Latch. What is the difference between this gated latch and the previous basic latches?



A gated D latch only has 1 input variable (besides the clock) and has a clock signal that is consistent, whereas the basic latches has two inputs that determine the output


D Latch Screenshots:
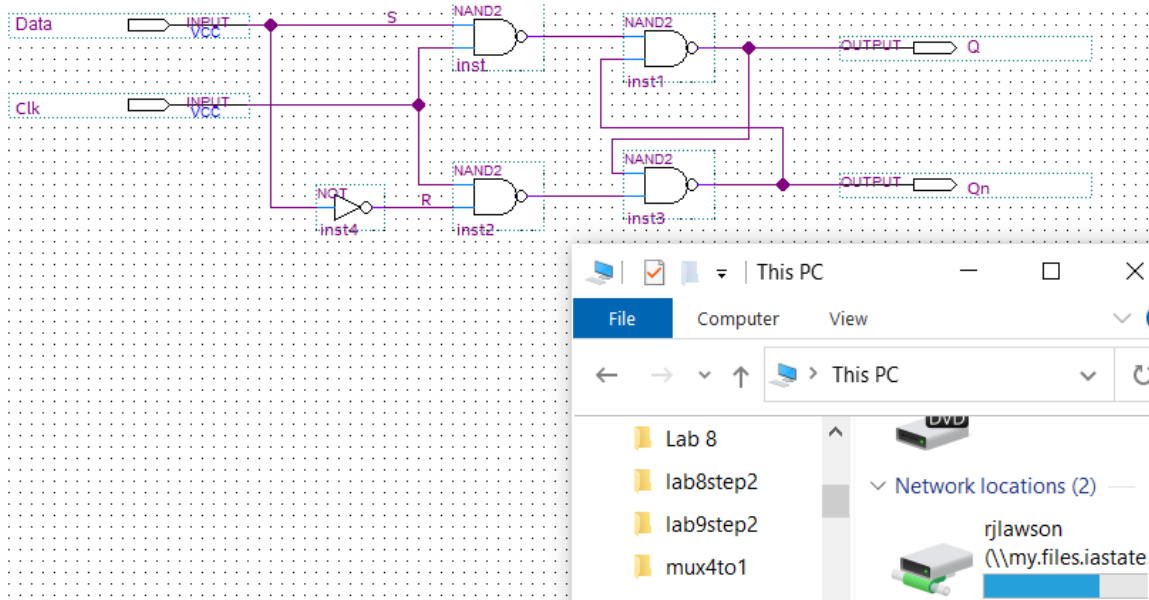
<<<Insert a screenshot of your D latch here>>>




Lab 9 Answer Sheet
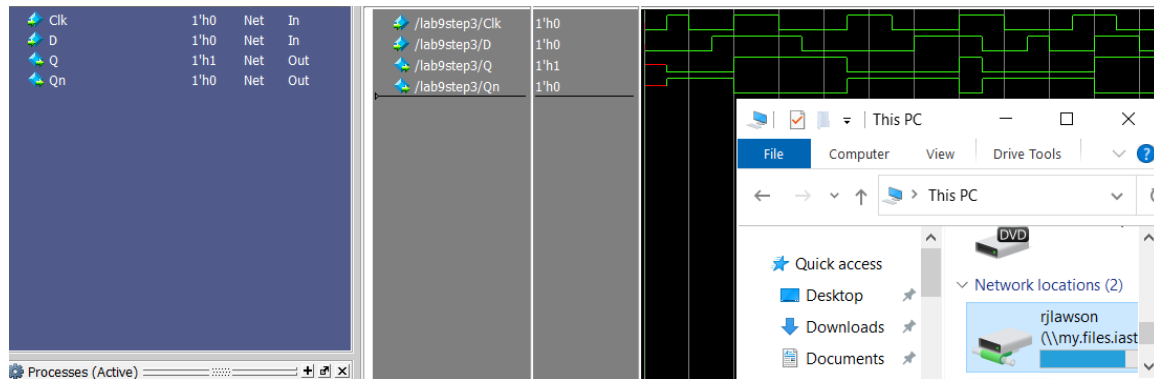
<<< Insert a screenshot of your waveform for your D latch here>>>




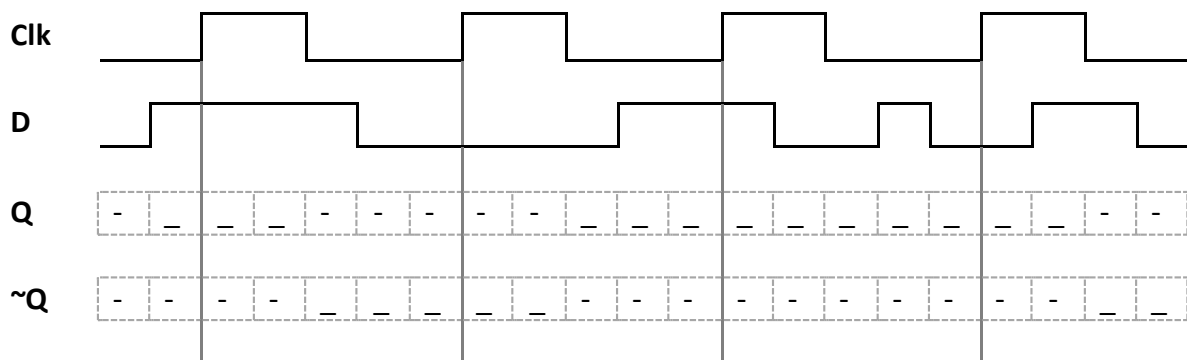4.0 Complete the timing diagram below for your Negative-Edge-Triggered D Flip-Flop.




Negative Edge D Flip-Flop Screenshots:

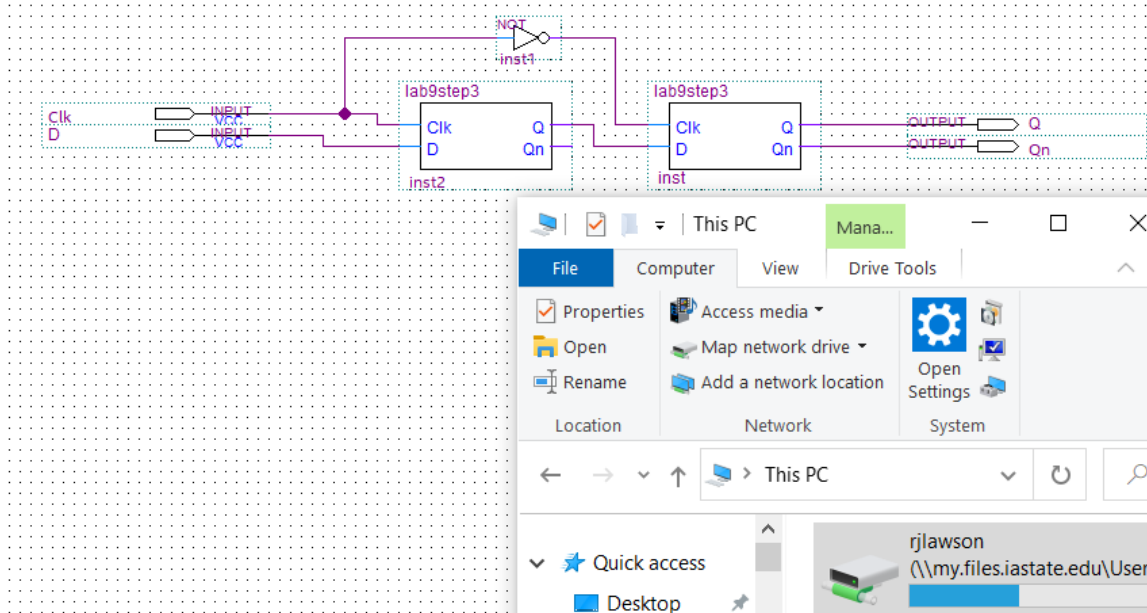
<<<Insert a screenshot of your Neg. Edge DFF here>>>


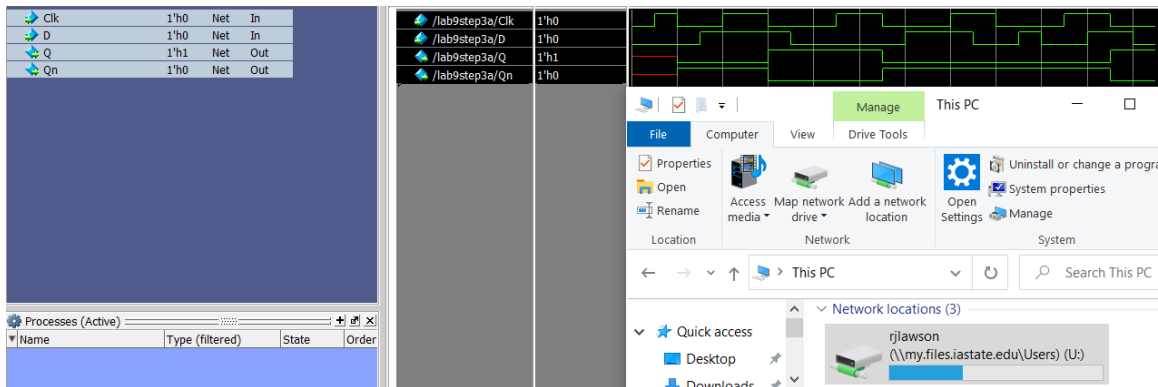
<<< Insert a screenshot of your Neg. Edge DFF waveform here>>>




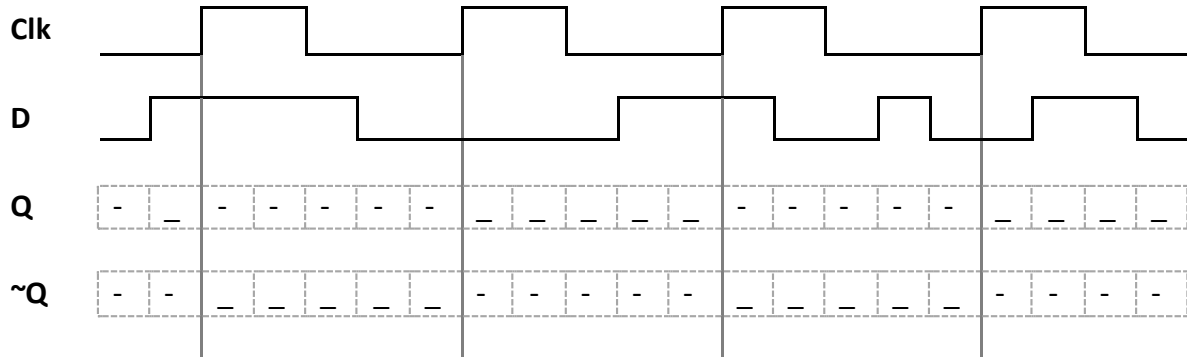Complete the timing diagram below for your Positive-Edge-Triggered D Flip-Flop.



Positive Edge D Flip-Flop Screenshots:
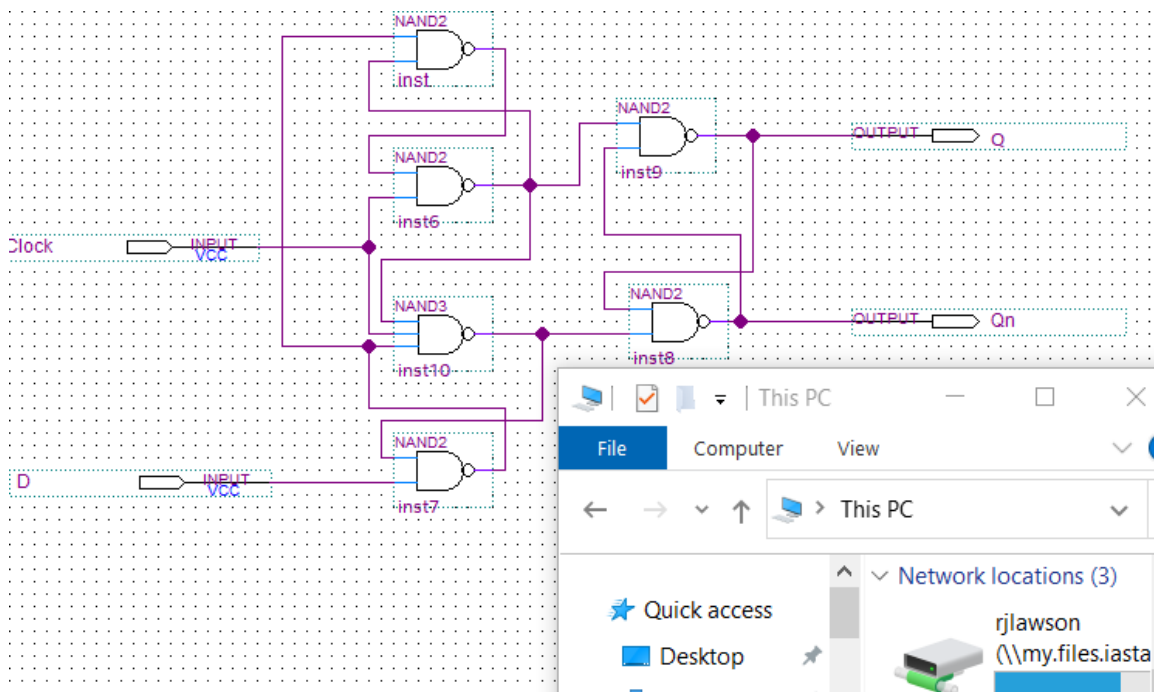
<<<Insert a screenshot of your Pos. Edge DFF here>>>



<<< Insert a screenshot of your Pos. Edge DFF waveform here>>>

