Name and Student ID:Riley Lawson rjlawson@iastate.edu Lab Section: 6

Date: 8/25/2020

PRELAB:

Q1. Fill in the Truth Table below for an AND gate:

Α	В	С
0	0	0
0	1	0
1	0	0
1	1	1

Q2. What does the .bdf file extension stand for?

Block Design Format

LAB: 2.0 Fill in the Truth Table for *lab1step1*:

Α	В	С
0	0	
0	1	
1	0	
1	1	

Logic Expression:	

4.0 Fill in the Truth Table for *lab1step2*:

W	Х	Υ	Z

0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

4.0 Fill in the Truth Table for *lab1step3*:

Α	В	С	F

Logi	c Expression	1:	