

Name and Student ID: Riley Lawson rjlawson@iastate.edu Lab Section: 6

Date: 8/25/2020

PRELAB:

Q1. Fill in the Truth Table below for an AND gate:

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Q2. What does the .bdf file extension stand for?

Block Design Format

LAB:

2.0 Fill in the Truth Table for *lab1step1*:

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Logic Expression: $AB = C$

4.0 Fill in the Truth Table for *lab1step2*:

W	X	Y	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Logic Expression: $\neg wx\neg y + w\neg x\neg y + wx y = z$

4.0 Fill in the Truth Table for *lab1step3*:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Logic Expression: $\neg A\neg BC + \neg ABC + A\neg BC + AB\neg C = F$