

Name and Std ID: Riley Lawson **Lab Section:** 6

Date: 10/8/2020

Submission Instructions:

Prelab:

1. Complete the prelab
2. Submit this report with the prelab completed to Canvas before your lab starts

Lab:


1. Complete the lab according to the instructions
2. Take screenshots of your ModelSim waveform (note: to receive points your NetID has to be present in the screenshot) and insert them into this document.
3. Include screenshots of any related block design files or Verilog files in the report
4. Complete this report and reupload it to Canvas

PRELAB:

Q1. Add the following numbers then write them in decimal:

| Binary numbers to add a3 a2 a1 a0 + b3 b2 b1 b0 | Binary result C0 S3 S2 S1 S0 | Decimal conversion N2 N1 (X3 X2 X1 X0) (X3 X2 X1 X0) |
|--|---|---|
| 1001 + 0111 | 10000 | 16 |
| 1011 + 1001 | 010100 | 20 |
| 1110 + 0101 | 010011 | 19 |
| 0010 + 1110 | 10000 | 16 |
| 1101 + 1011 | 011000 | 24 |

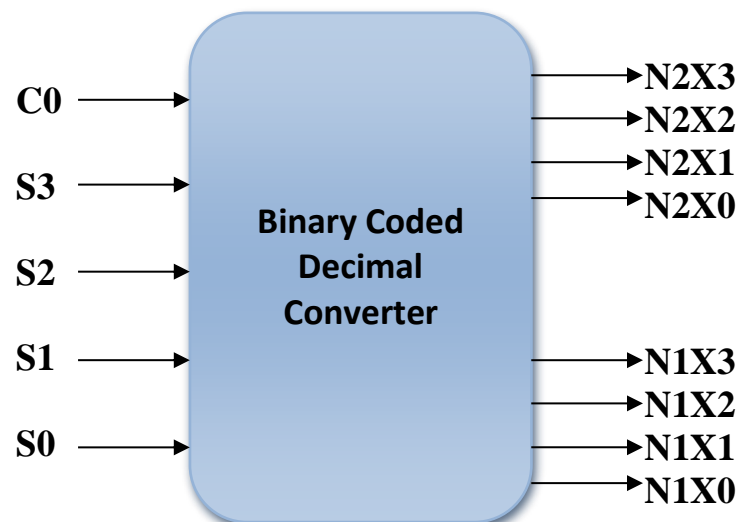Q2. Consider the five-bit binary result (C0, S3, S2, S1, S0) representation in the table above. We would like to represent each combination as its equivalent in two decimal digits, each of which can be represented in binary as shown in the following table. Finish filling in the following truth table.



Lab 6 Answer Sheet

| C0 | S3 | S2 | S1 | S0 | Decimal | N2X3 | N2X2 | N2X1 | N2X0 | N1X3 | N1X2 | N1X1 | N1X0 |
|----|----|----|----|----|---------|------|------|------|------|------|------|------|------|
| 0 | 0 | 0 | 0 | 0 | 0 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 2 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 3 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 4 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 5 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 6 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 7 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 8 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 9 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 2 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 3 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 4 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 5 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 6 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 7 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 8 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 9 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 2 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 2 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 2 2 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 2 3 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 2 4 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 2 5 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 2 6 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 2 7 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 2 8 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 2 9 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 3 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 3 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |

Q3. Find the logic expressions for N2X3, N2X2, N2X1, N2X0, N1X3, N1X2, N1X1, and N1X0 as a function of C0, S3, S2, S1 and S0:

$$N2X3 = 0;$$

$$N2X2 = 0;$$

$$N2X1 = (c0 \& s2) \mid (c0 \& s3)$$

$$N2X0 = (\sim c0 \& s3 \& s1) \mid (\sim c0 \& s3 \& s2) \mid (c0 \& s3 \& \sim s2) \mid (s3 \& s2 \& s1);$$

$$N1X3 = (\sim c0 \& s3 \& \sim s2 \& \sim s1) \mid (c0 \& \sim s3 \& \sim s2 \& s1) \mid (c0 \& s3 \& s2 \& \sim s1);$$


$$N1X2 = (\sim c0 \& \sim s3 \& s2) \mid (\sim c0 \& s2 \& s1) \mid (s1 \& \sim c0 \& s2) \mid (c0 \& s3 \& \sim s2);$$

$$N1X1 = (\sim c0 \& \sim s3 \& s1) \mid (\sim c0 \& s3 \& s2 \& \sim s1) \mid (c0 \& \sim s3 \& \sim s2 \& \sim s1) \mid (\sim s3 \& s2 \& s1) \mid (c0 \& s3 \& \sim s2 \& s1);$$

$$N1X0 = (s0)$$

Q4. Write the verilog code for the Binary Coded Decimal Converter from **Section 3.3** using the assign statement.

```
module binary_decimal_converter(s0, s1, s2, s3, c0, Z2, Y2, X2, W2, Z, Y, X, W);  
    input s0, s1, s2, s3, c0;  
    output Z2, Y2, X2, W2, Z, Y, X, W;  
  
    assign Z2 = 0;  
    assign Y2 = 0;  
    assign X2 = (c0 & s2) | (c0 & s3);  
    assign W2 = (~c0 & s3 & s1) | (~c0 & s3 & s2) | (c0 & s3 & ~s2) | (s3 & s2 & s1);  
  
    assign Z = (~c0 & s3 & ~s2 & ~s1) | (c0 & ~s3 & ~s2 & s1) | (c0 & s3 & s2 & ~s1);  
    assign Y = (~c0 & ~s3 & s2) | (~c0 & s2 & s1) | (s1 & ~c0 & s2) | (c0 & s3 & ~s2);  
    assign X = (~c0 & ~s3 & s1) | (~c0 & s3 & s2 & ~s1) | (c0 & ~s3 & ~s2 & ~s1) | (~s3 & s2 & s1) | (c0 & s3 & ~s2 & s1);  
    assign W = (s0);  
  
endmodule
```

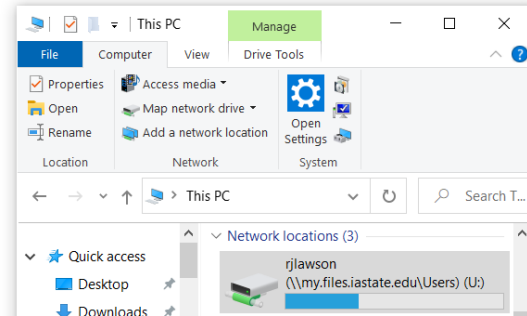

LAB:

Hardware demonstrates a good design.

<<Insert a screenshot of your BDF file here>>

Lab 6 screenshots:

To get full points, replace this screenshot with your results

- To find your NetID, open the start menu and search for "This PC". Then scroll down to reveal your NetID

