

Name and Std ID: Riley Lawson rjlawson Lab Section: 6

Date: 10/15/2020

Submission Instructions:

Prelab:

1. Complete the prelab
2. Submit this report with the prelab completed to Canvas before your lab starts

Lab:

1. Complete the lab according to the instructions
2. Take screenshots of your ModelSim waveform (note: to receive points your NetID has to be present in the screenshot) and insert them into this document.
3. Include screenshots of any related block design files or Verilog files in the report
4. Complete this report and reupload it to Canvas

PRELAB:

Q1. Before you fill in the answers to this prelab make sure that you understand binary arithmetic, especially signed number representation (2's Complement) and overflow in arithmetic addition and subtraction. Do the following arithmetic operations and write down the expected sum, carry and overflow:

In case of subtraction, since we are doing a 2's Complement addition Cout is the carryout of the adder.

Binary numbers to add/subtract	Sum	Cout	Overflow
1011 – 0110	0101	1	1
1001 - 0010	0111	1	1
0001 + 0111	1000	0	1
1100 + 0110	0010	1	0
0011 – 1101	0110	0	0
0101 + 1011	0000	1	0

Q2. Complete the truth table for a full adder:

X	Y	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Q3. Complete the assignment expressions for S and Cout below:

```
module FA (X, Y, Cin, Cout, S);  
input Cin, X, Y;  
output Cout, S;  
assign S = (expression for S);  
assign Cout = (expression for Cout);
```


Expression for S: $\neg X \neg Y \text{Cin} + \neg X Y \text{Cin} + X \neg Y \text{Cin} + XY \text{Cin}$

Expression for Cout: $\neg X Y \text{Cin} + X \neg Y \text{Cin} + XY \neg \text{Cin} + XY \text{Cin}$


Lab 7 Answer Sheet

LAB:
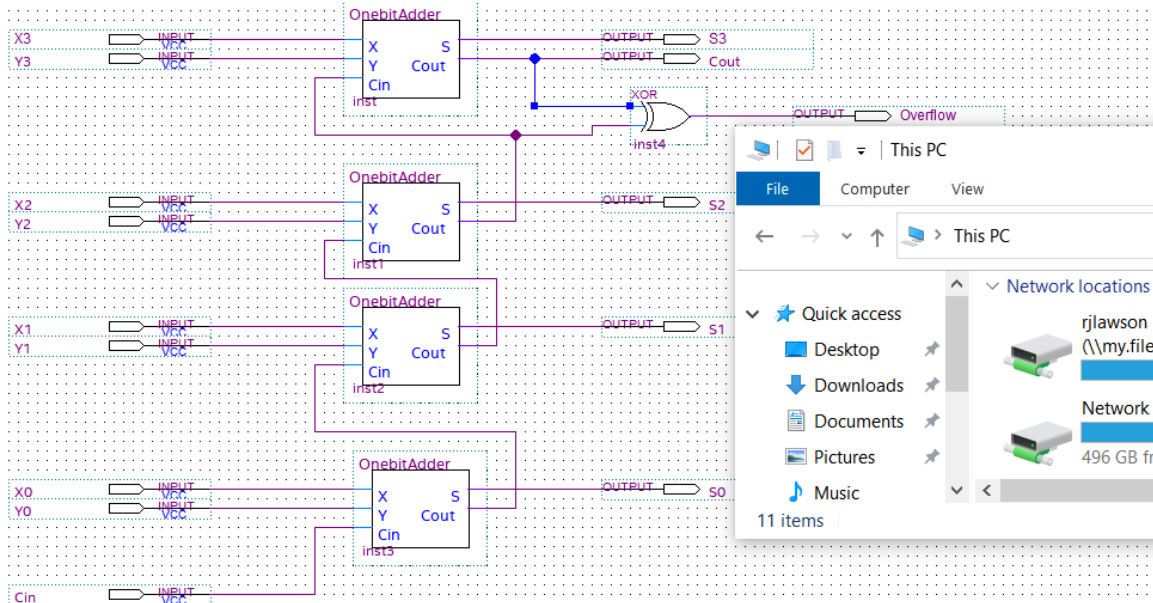
<<Insert a screenshot of your BDF file (adder_4bit.bdf) here>>


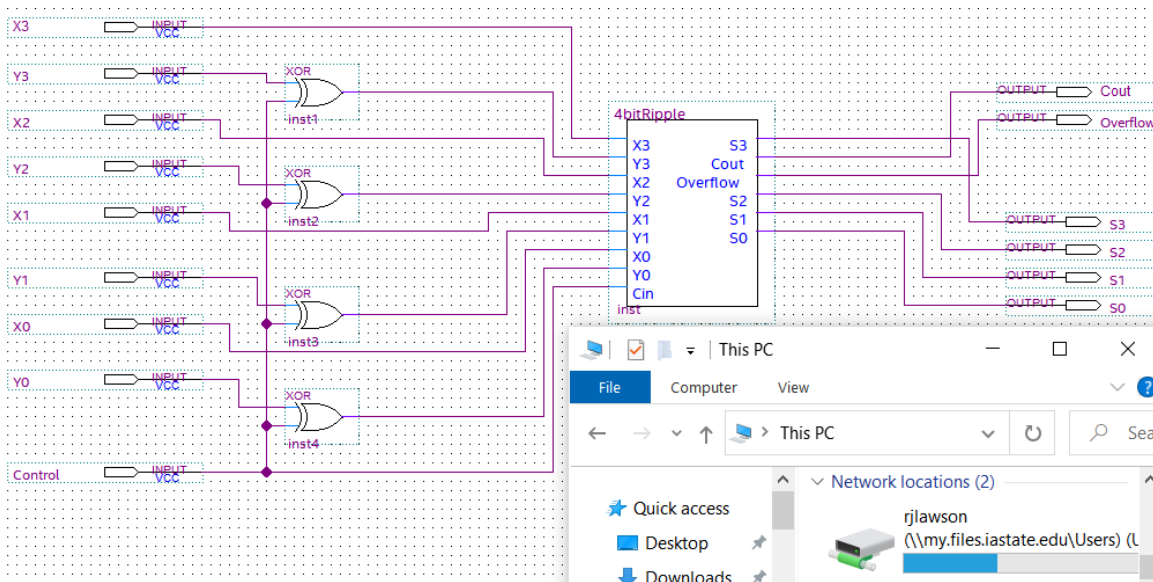
<<Insert a screenshot of your BDF file (add_sub.bdf) here>>



Lab 7 Answer Sheet

```
force -freeze Control 1 0
run
force -freeze X3 0 0
force -freeze X2 0 0
force -freeze X1 0 0
force -freeze X0 1 0
force -freeze Y3 0 0
force -freeze Y2 1 0
force -freeze Y1 1 0
force -freeze Y0 1 0
force -freeze Control 0 0
run
force -freeze X3 1 0
force -freeze X2 1 0
force -freeze X1 0 0
force -freeze X0 0 0
force -freeze Y3 0 0
force -freeze Y2 1 0
force -freeze Y1 1 0
force -freeze Y0 0 0
force -freeze Control 0 0
run
force -freeze X3 0 0
force -freeze X2 0 0
force -freeze X1 1 0
force -freeze X0 1 0
force -freeze Y3 1 0
force -freeze Y2 1 0
force -freeze Y1 0 0
force -freeze Y0 1 0
force -freeze Control 1 0
run
force -freeze X3 0 0
force -freeze X2 1 0
force -freeze X1 0 0
force -freeze X0 1 0
force -freeze Y3 1 0
force -freeze Y2 0 0
force -freeze Y1 1 0
force -freeze Y0 1 0
force -freeze Control 0 0
run
```

<<Insert a screenshot or copy your DO file here>>

```
|add wave -position insertpoint \  
sim:/X3 \  
sim:/X2 \  
sim:/X1 \  
sim:/X0 \  
sim:/Y3 \  
sim:/Y2 \  
sim:/Y1 \  
sim:/Y0 \  
sim:/Control \  
sim:/S3 \  
sim:/S2 \  
sim:/S1 \  
sim:/S0 \  
sim:/Cout \  
sim:/Overflow  
force -freeze X3 1 0  
force -freeze X2 0 0  
force -freeze X1 1 0  
force -freeze X0 1 0  
force -freeze Y3 0 0  
force -freeze Y2 1 0  
force -freeze Y1 1 0  
force -freeze Y0 0 0  
force -freeze Control 1 0  
run  
force -freeze X3 1 0  
force -freeze X2 0 0  
force -freeze X1 0 0  
force -freeze X0 1 0  
force -freeze Y3 0 0  
force -freeze Y2 0 0  
force -freeze Y1 1 0  
force -freeze Y0 0 0  
force -freeze Control 1 0  
run  
force -freeze X3 0 0  
force -freeze X2 0 0  
force -freeze X1 0 0  
force -freeze X0 1 0  
force -freeze Y3 0 0  
force -freeze Y2 1 0
```

Lab 7 Answer Sheet

<<< Insert a screenshot of your DO file waveform>>>

